

Digital Test

Name

Date

Draw the appropriate symbol for the following terms:

1. NPN Transistor _____

2. Zener Diode _____

3. NAND Gate, 2 input _____

4. Variable Resistor _____

5. Full Wave Bridge _____

6. Transformer _____

7. Inductor _____

8. PNP Transistor _____

9. Fuse _____

10. Circuit Breaker _____

Digital Test


_____ Name

_____ Date

Provide the following conversions:

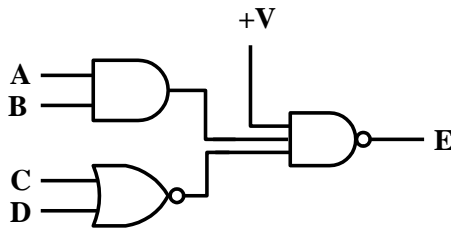- 11. 1000 pico farad to _____ microfarad
- 12. 0.100 volts to _____ milli volts
- 13. 0.001 volts to _____ milli volts
- 14. 0.001 kΩ to _____ ohms
- 15. 0.01 μ sec to _____ nano sec

Provide the correct output for the given Inputs in the following circuit (assume positive logic):




16.	A B C D	E
	0 0 0 1	_____
17.	1 1 0 0	_____
18.	1 0 1 0	_____

Digital Test

_____ Name _____

_____ Date _____

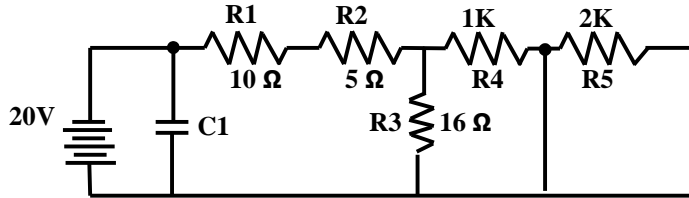19. Determine the voltage drop for the following:



20. R5 _____

R2 _____

C1 _____

R1 _____

Complete the following formulas:

21. Power = _____ X Voltage


22. Current = _____ ÷ Voltage

23. Voltage = Current X _____

Digital Test

Name


Date

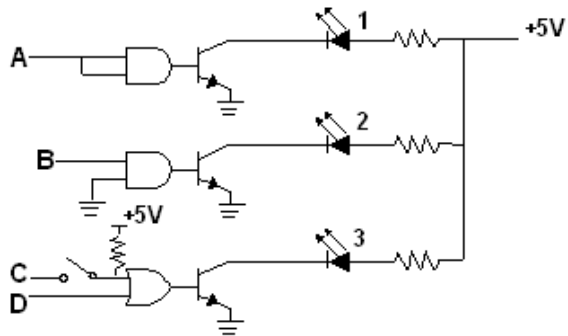

	A	B	C	D	1	2	3
24.	L	H	L	L			
25.	H	L	H	L			
26.	L	H	L	H			
27.	H	H	L	H			

28. Draw a latch using 2 dual input NAND gates. Label \bar{R} , \bar{S} , Q and \bar{Q} .

29. Describe the circuit listed below.

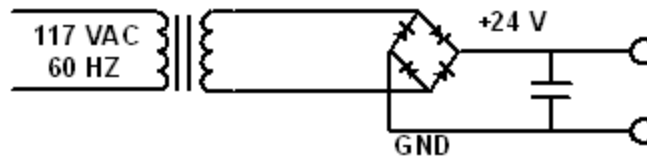


30. What RMS voltage would be required at the transformer secondary to provide specified output of 7 volts (on question 29)?

31. What does the band on Diode packages indicate?

Digital Test

_____ **Name** _____ **Date**

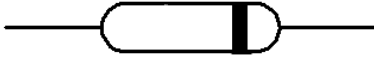

32. To measure current through a resistor, an ammeter must be connected in _____

33. To measure a voltage across a resistor, a voltmeter must be connected in _____

What is the typical forward voltage drop of the following devices for operating conditions usually encountered?

34. Silicon signal Diode _____

35. LED _____

36. SCR (Anode to Cathode) _____

37. Germanium signal Diode _____

38. Silicon small signal transistor VCD SAT. _____

39. Given binary 1001 1110, convert to hexadecimal _____

40. Given hexadecimal FC0B, convert to binary equivalent _____

41. According to the diagram below, how long will it take V_{c1} to reach 63.2% Of V_{cc} or 6.32V? _____

Digital Test

Name _____

Date _____

